
Electrical Take-Home Project -

Remote Load Switch

For the following prompts, please create schematic-level designs that implement the requested circuits. You may specify any number of DC power sources that you need for the design without drawing the regulators supplying them.

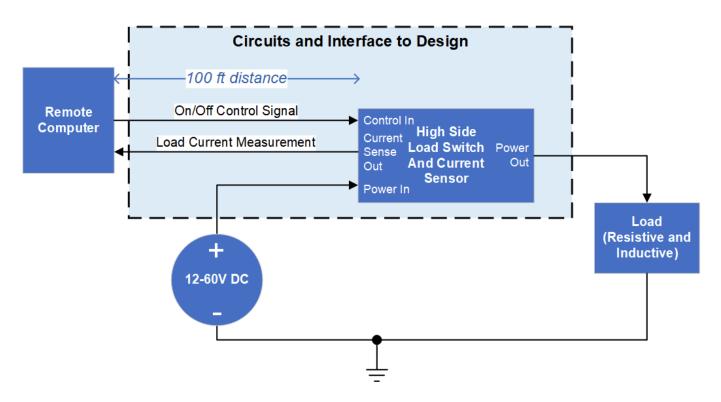For this project you are asked to create a high side load switch and current sensor circuit that can be controlled by a remote computer up to 100 feet away. This design should switch 12-60V DC power into a load, measure the load current, and report it back to the remote computer.



More detailed requirements for the load switch, current sensing, and remote interface are provided on the following page

Load Switch

Design a circuit for a high-side load switch capable of switching 12-60 VDC into an inductive load (L < 5mH) at currents of up to 10A. The switch shall be capable of operating continuously, but may be cycled on and off at a frequency lower than 1 Hz.

Load Current Measurement

The circuit shall measure and report the load current with a resolution of 10mA to the remote computer at a rate of 100Hz. Note that the load current may contain higher frequency content than DC. For purposes of this problem, only unidirectional current sensing is needed.

Remote Computer Interface

The load switch and current sensing circuits need to be interfaced to a remote computer that may be located up to 100 feet away from the circuits. Please design an interface using technologies of your choice to both send the on/off command to the switch circuit and report out the measured load current to the computer. These interfaces may be shared or separate.


General Environments


This circuit should be considered to be deployed into a vehicle environment (like an aircraft or road vehicle). These environments may include


- -40 to +70°C ambient temperatures
- Standard atmospheric pressure
- Some potential exposure to conducted and radiated electromagnetic interference
- Moderate mechanical shock and vibration


Deliverables

- Written document describing your design choices and any analysis that supports them.
 - Present your work such that another engineer can understand your design with the material provided.
- Schematics containing the requested load switch, current sensing, and interface circuits
 - Note: The schematics can be done either in CAD or by hand
- Bill of materials (BOM)
 - For critical components (i.e. IC's/transistors) specify part numbers
 - Passive components can be specified by value and other key characteristics that you think would be necessary to adequately describe the component

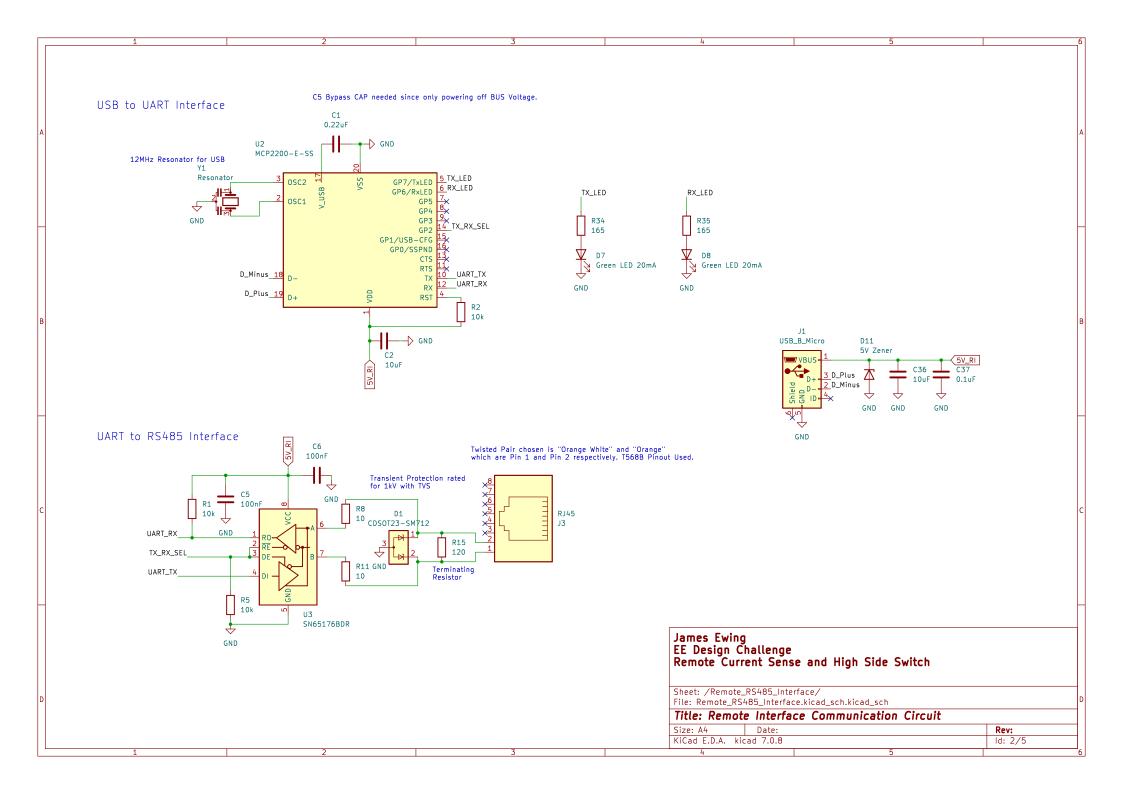

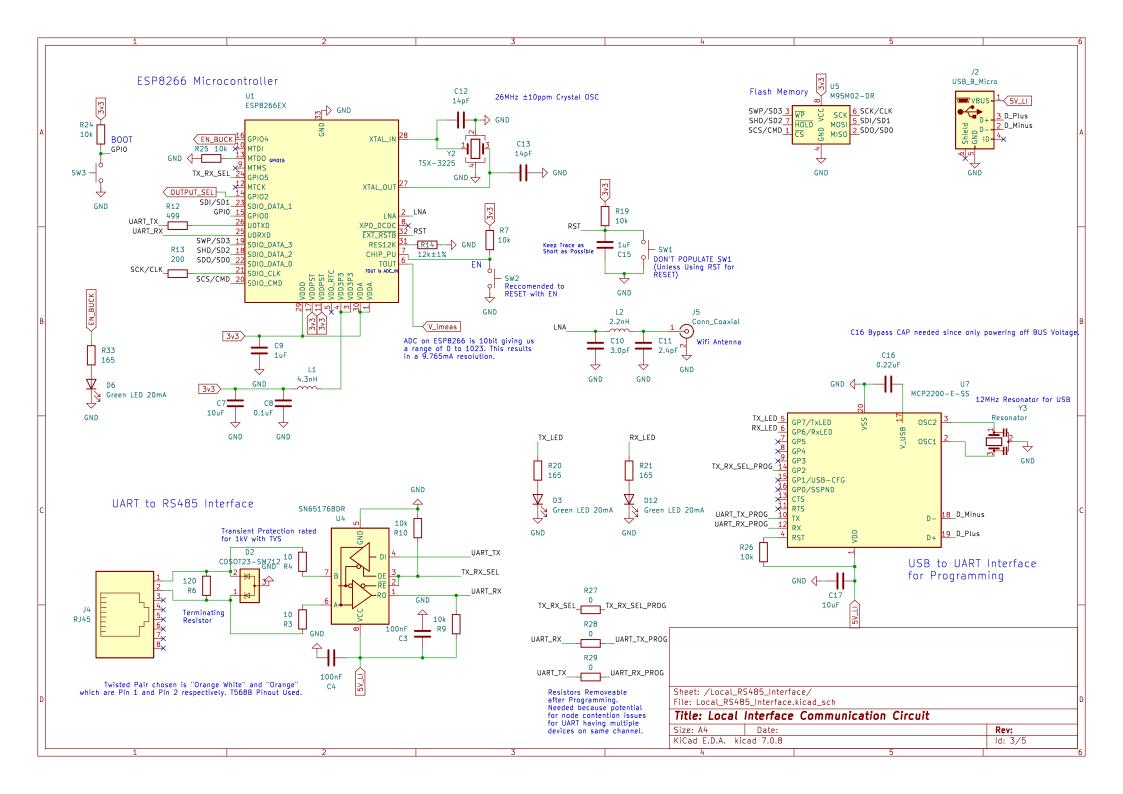

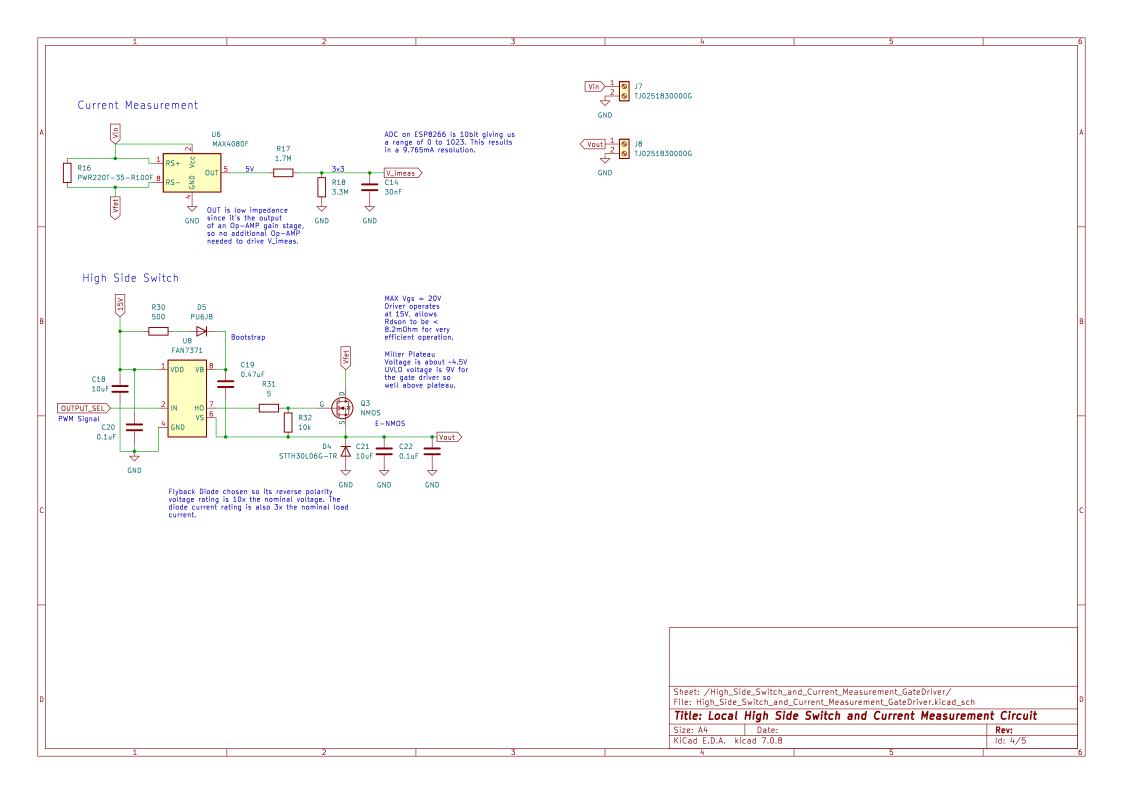

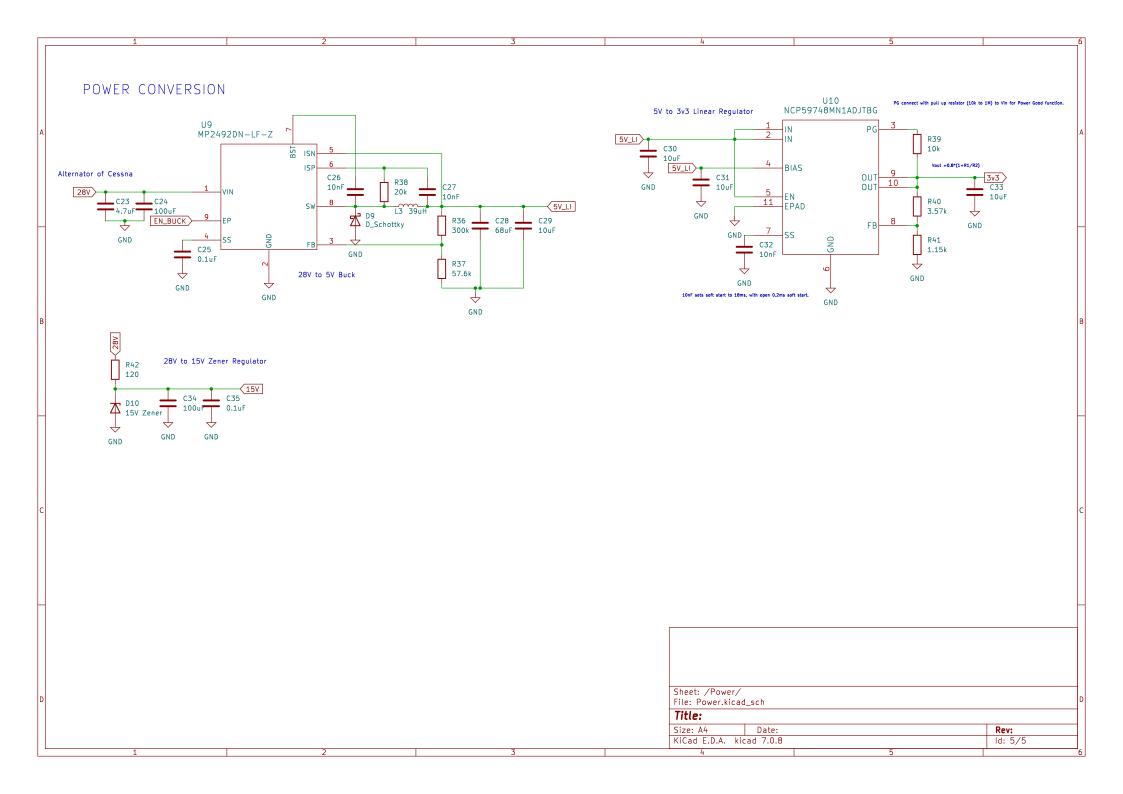

Remote RS485	Interface						
d Designate	or Footpri	int Quantity	Designation	Description	Purchase Link	Data Sheet	
1 U3, U4	SOP 8		2 SN65176BDR	RS485 Transceivers	https://www.digil	https://mm.digike	Link
2 J3,J4	RJ45		2	Shielded RJ45 Connectors	https://www.digil	https://app.adam	Link
3 R1, R2, F	3, R4 Imperia	al: 0402	4 10 ohm	RS485 Res Pulse Proof Thick Film	https://www.digil	https://www.te.co	Link
4 R5, R6	Imperia	al: 0402	2 120 ohm	120 ohm, RS485 Term Res			
5 R7, R8, F	89, R10, R15 Imperia	al: 0402	4 10k	10k ohm Res, UART-RS485			
6 D1, D2	SOT23		2 TVS CDSOT23-S	SM712 TVS Diode, RS485	https://www.digil	https://www.bou	Link
7 C1, C2, C	3, C4 Imperia	al: 0402	4 100nF	Ceramic Cap, RS485			
8 U5	USB to	UART	2 MCP2200-I/SO	USB to UART Interface	https://www.mou	https://www.mou	Link
9 C5	Imperia	al: 0402	1 0.22uF	Bypass CAP	https://www.digil	https://mm.digike	Link
10 C6	Imperia	al: 0402	1 10uF	Bus CAP (Can't be more than 10uF)	https://www.digil	https://www.mur	Link
11 J1, J2	Micro-U	JSB	1	USB Connection to Rem PC			
12 Y1	3 Pads	(Dim Given)	2 12MHz 33pF	Ceramic Resonator	https://www.digil	https://www.mura	Link
13 R11	Imperia	al: 0402	1 10k	RES for RESET			
14 D11			1 5V Zener	Clamp Zener			
ocal RS485 Int	erface						
Designato	or Footpri	nt Quantity	Designation	Description	Purchase Link	Data Sheet	
1 U1	ESP82	66 (Slave)	1				
2 R12	Imperia	al: 0402	1 499 ohm	UARTRX Res			
3 R13	Imperia	al: 0402	1 200 ohm	SDIO_CLK Res			
4 R14	Imperia	al: 0402	1 12k±1%	RES12K Res			
5 C7	Imperia	al: 0402	1 10uF				
6 C8	Imperia	al: 0402	1 0.1uF				
7 C9	Imperia	al: 0402	1 1uF				
8 C10	Imperia	al: 0402	1 3.0pF				
9 C11	Imperia	al: 0402	1 2.4pF				
10 J5	SMA		1 Wifi SMA Coax C	Conn			
11 U2	S08N		1 8266 Flash Mem	ory M95M02-DR	https://www.digil	https://www.st.co	Link
12 C12, C13	Imperia	al: 0402	2 14pF	Crystal OSC Caps			
13 Y2	4 Pads	(Custom)	1 26Mhz ±10ppm	Crystal Oscillator	https://www.digil	https://support.e	Link
14 L1	Imperia	al: 0603	1 4.3nH				
15 L2	Imperia	al: 0603	1 2.2nH				
ligh Side Switc	h and Current Sense						
Designate	or Footpri	int Quantity	Designation	Description	Purchase Link	Data Sheet	Notes
1 U6	8SOIC		1 MAX4080	High Side Current Sensor	https://www.digil	https://www.anal	Link
2 R17	Imperia	al: 0402	1 1.7M				
3 R18	Imperia	al: 0402	1 3.3M				
4 C14	Imperia	al: 0402	1 30nF				
5 R16	THT		1 0.1ohm, 35W	Current Sense Resistor	https://www.new	https://www.farn	Link

6	Q1	TO-252	1	AOD66920	Load Switch	https://www.digik htt	ps://aosmd.co	Link
7	D3	D2PAK	1	STTH30L06G-TR	Flyback Diode	https://www.digik htt	ps://mm.digike	Link
8	J6, J7	Screw Terminal Conn	2	300VAC 20A	TJ0251830000G	https://www.digik htt	p://www.anyte	Link
9	U5		1	FAN73711	Gate Driver	https://www.digik htt	ps://www.onse	Link
10	C17		1	0.47uF	Bootstrap Capacitor	https://www.digik htt	ps://calchip.cc	Link
11	R19		1	500 ohm	Bootstrap Resistor	https://www.digik htt	ps://fscdn.rohi	Link
12	D4		1	PU6JB	Bootstrap Diode	https://www.digik htt	ps://www.taiwa	Link
13	C18, C21		2	10uF	Bypass Caps			
14	C20, C22		2	0.1uF	Bypass Caps			
15	R20		1	5ohm	Gate Resistor			
owe	Conversion							
d	Designator	Footprint	Quantity	Designation	Description	Purchase Link Da	ıta Sheet	Notes
1	U9	8SOIC	1	MP2492DN-LF-Z	28V to 15V Buck	https://www.digik htt	ps://www.mon	Link
2	C23		1	4.7uF				
	C24		1	100uF				
	C25, C35, C37		3	0.1uF				
	C26, C27, C32		3	10nF				
	C28		1	68uF				
	C29, C30, C31, C33, C36		5	10uF				
	R36		1	300k				
	R37		1	57.6k				
	R38		1	20k				
	D9		1	Schottky 15V Vbr				
	R39		1	10k				
	R40		1	3.57k				
	R41		1	1.15k				
				NODEOZAONANIA AD ITDO	5V to 3v3 Linear Regulator	https://www.digik.htt	ne-//www.ones	Link
	U10		1	NCP59748MN1ADJTBG	3V to 3V3 Linear Regulator	TILLPS.//WWW.uigin IIIL	D3.//WWW.01136	LIIIK
	U10 D10			3SMAJ5929B-TP	15V Zener	https://www.digik	•	
			1		-		•	